

Transmission Line and Voltage Standing Wave Ratio

Feza Turgay Celik


Dr. Yanki Aslan

f.t.celik@tudelft.nl

Microwave Sensing, Signals and Systems (MS3) Group
Delft University of Technology

Circuit and transmission line theory

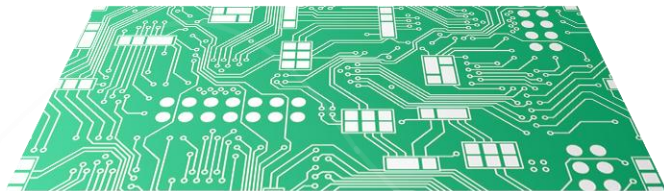
Low frequency: Wavelength is much larger than the circuit size




Circuit theory




Quasi-static

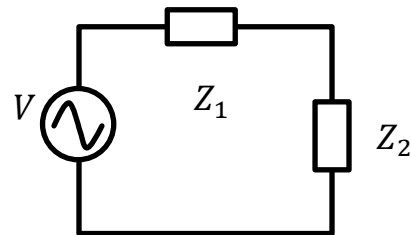

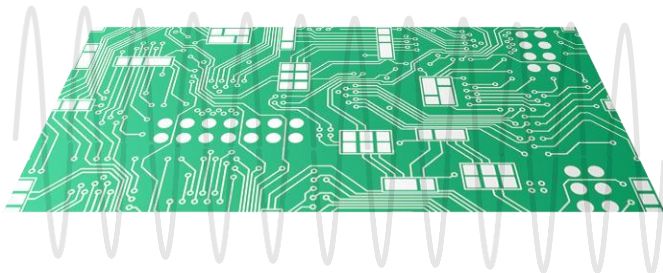High frequency: Wavelength is much smaller than circuit size




Transmission line theory

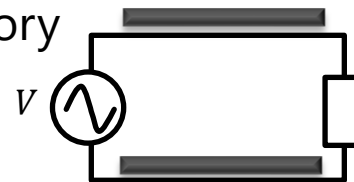

Different phases at different locations in the circuit

Unlike in circuit theory, the **length** of a transmission line is important to determine voltage and current

Transmission lines

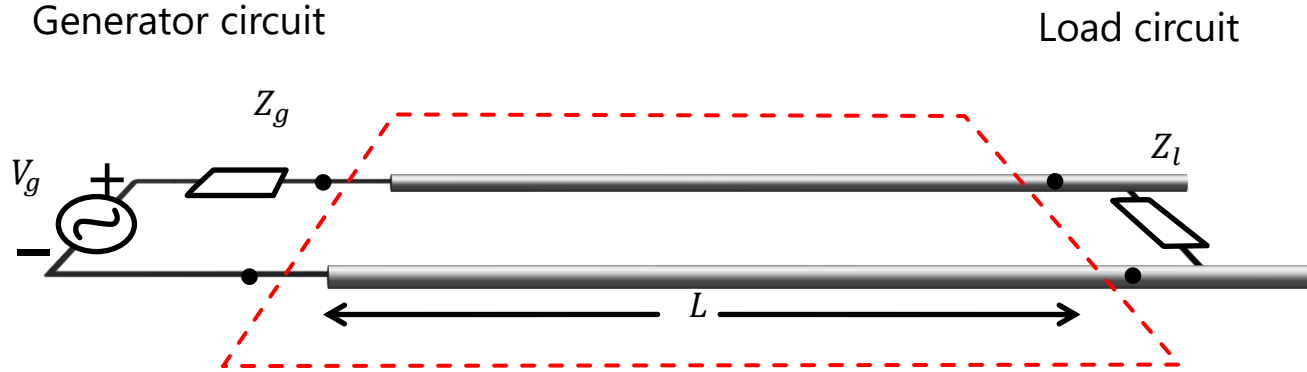

A transmission line is a two-port network connecting a generator circuit at the sending end to a load at the receiving end.

- It is a structure to carry alternating current and electromagnetic waves from one place to another
- E.g.: connecting radio transmitters and receivers with their antennas, distributing cable television signals, and computer network connections, etc.

Outline

1. Basics of travelling wave

1. Current and Voltage waves in Transmission Lines
2. Introduction on Characteristic impedance, load and mismatch terms


2. Background information

1. Intro to Transmission Line (TL)
2. Intro to Standing wave

3. How can we measure mismatch and find load?

1. Voltage Standing Wave Ratio
2. Load Calculation

1. Basics of travelling wave

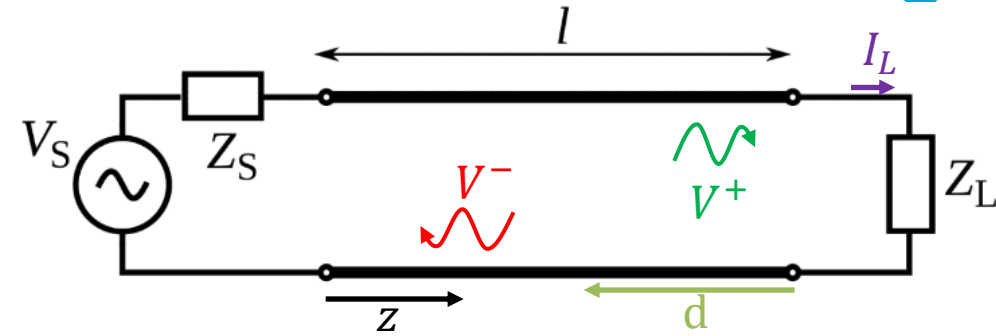

- One of the mathematical ways to represent waves are the complex exponentials. In our notation $e^{-\gamma z}$ denotes forward propagating wave.
- $\gamma = \alpha + j\beta$ where α quantifies loss terms while β determines propagation properties
- Waves in TL can be decomposed as **incident** (forward going), and **reflected** (backward going)
- TL's have a characteristic impedance (Z_{ch}) determined by dimensions of the TL and the dielectric material (independent of length). The voltage and current waves within the TL scales with Z_{ch}

$$V(z) = V^+ e^{-\gamma z} + V^- e^{+\gamma z} \quad \text{Voltage wave}$$

We can write voltage at $z=l$ or $d=0$

$$V_L = \underbrace{V^+ e^{-\gamma l}}_{V_L^+} + \underbrace{V^- e^{+\gamma l}}_{V_L^-}$$

$$V(d) = V_L^+ e^{+\gamma d} + V_L^- e^{-\gamma d}$$

$$I_L = I_L^+ + I_L^- = \frac{V_L^+}{Z_{ch}} - \frac{V_L^-}{Z_{ch}}$$

$$I(d) = \frac{V_L^+ e^{+\gamma d} + V_L^- e^{-\gamma d}}{Z_{ch}} \quad \text{Current wave}$$

Introduction on Characteristic impedance, load and mismatch terms

Resistance against
applied voltage
(R)


+

Storage due to
change in applied
voltage
(X)



Impedance
or Load
 $Z_L = (R + jX)$

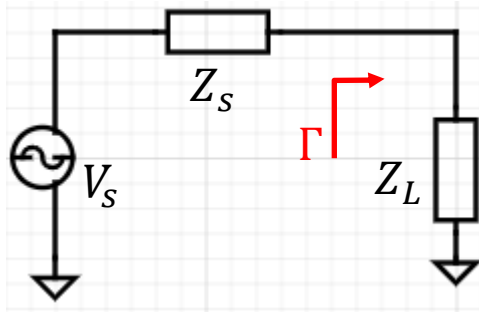- Frequency dependent due to X
- Complex number in general



Max. Power Transfer


$$Z_s = Z_L^*$$
$$P_{Load} = P_{gen}$$

Mismatch


$$Z_s \neq Z_L$$
$$\Gamma = \frac{Z_L - Z_s}{Z_L + Z_s} \quad P_{Load} = (1 - |\Gamma|^2) P_{gen}$$

2. Background Information

Coaxial transmission line

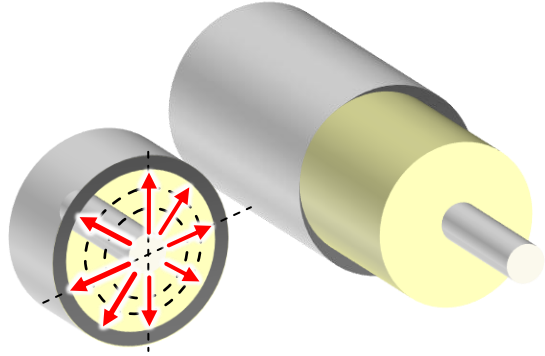

Rectangular waveguide

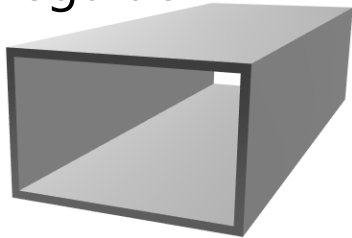

$$\gamma = \alpha + j\beta$$

Attenuation constant α (red)
Propagation constant $j\beta$ (green)

Transmission Line

$\beta \neq k_0$ due to dielectric

Waveguide

$\beta \neq k_0$ due to cutoff relation

$$\beta = w\sqrt{\mu_0\epsilon_0\mu_r\epsilon_r}$$

$$\lambda_g = \lambda_0 / \sqrt{\mu_r\epsilon_r}$$


Phase velocity

$$u_p = \frac{w}{\beta}$$

$$\beta = k_0 \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

$k_0 = \frac{2\pi}{\lambda_0}$ wave number, f_c cut-off
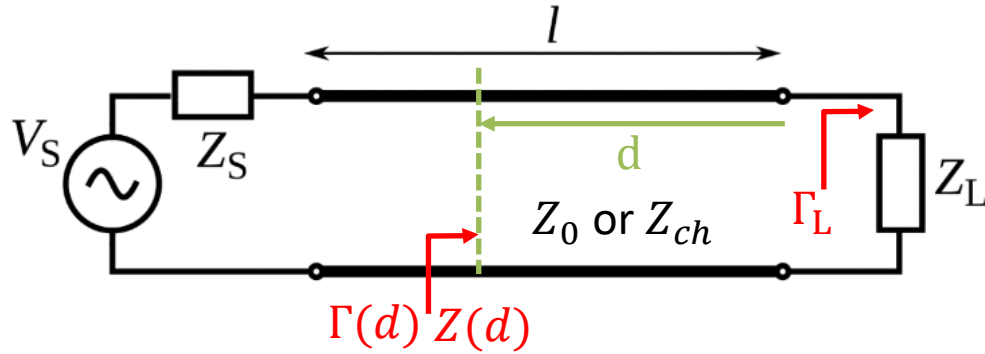
$$\lambda_w = \frac{\lambda_0}{\sqrt{1 - \left(\frac{\lambda_0}{2a}\right)^2}}$$




$$\Gamma(d) = \frac{Z(d) - Z_0}{Z(d) + Z_0} = \Gamma_L e^{-2\gamma d}$$

$$\gamma = \alpha + j\beta$$

$$Z(d) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)} \xrightarrow[\alpha = 0]{\text{lossless}} Z_{\text{lossless}}(d) = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)}$$

Standing Wave

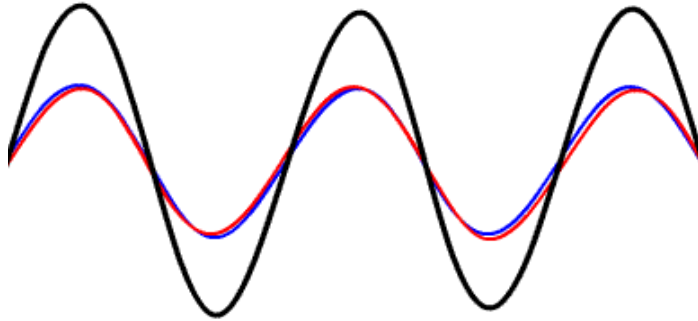


Incident, Reflected, Standing

A measure of how much standing waves are present is the Voltage standing wave ratio (VSWR)


$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

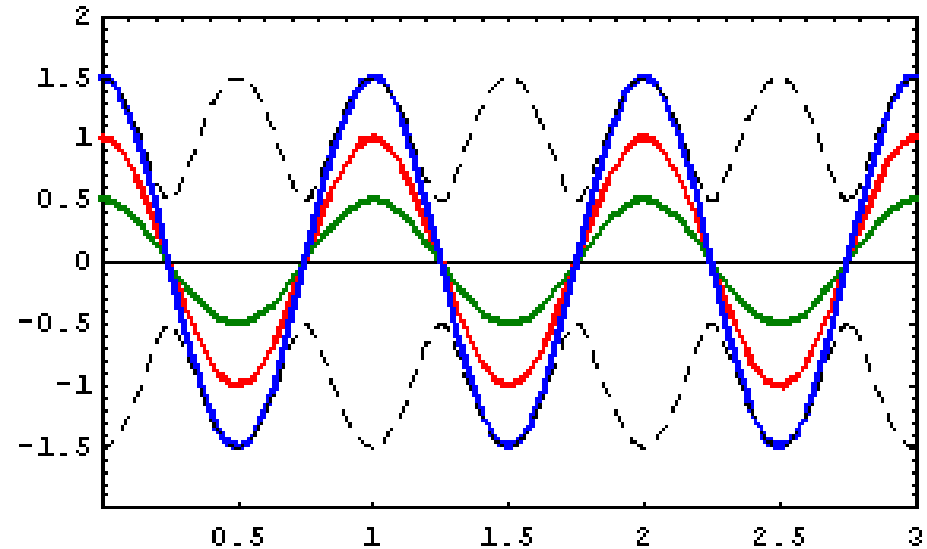If they don't have the same amplitude
Oscillate between a max and a min



Incident, Reflected, Standing

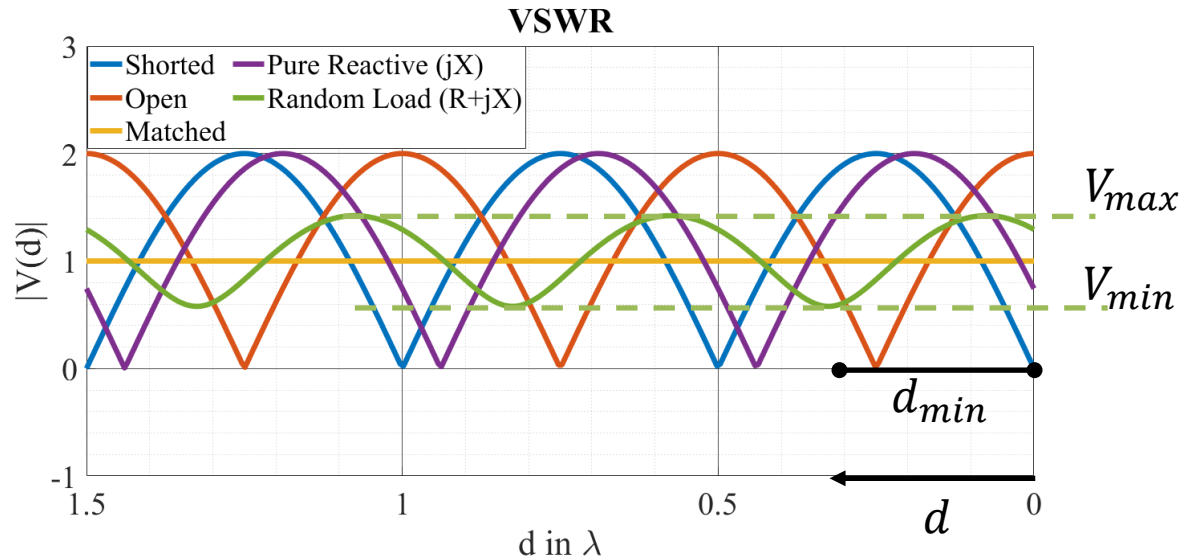3. How can we measure mismatch and find load?



$$VSWR (S) = \frac{V_{max}}{V_{min}} = \frac{1+|\Gamma|}{1-|\Gamma|}$$

- $1 \leq S < \infty$
- $|\Gamma_L| = 0$
Matched Load

 - $Z_L = 0$
Shorted Load

$|\Gamma_L| = 1$

 - $Z_L = \infty$
Open Load
 - $Z_L = jX$
Purely Reactive Load

How to calculate load by VSWR graph?

Assuming lossless TL we can express reflection coeff. As;

$$Z_L = Z_0 \frac{1-\Gamma_L}{1+\Gamma_L} \quad \text{and} \quad \Gamma_L = |\Gamma_L|e^{j\theta_L}$$

1. Determine $|\Gamma_L|$

$$S = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} \quad \text{yields} \quad |\Gamma_L| = \frac{S-1}{S+1}$$


2. Determine θ_L

At $d = d_{min}$ voltage reflected and voltage incident has π phase difference

$$\frac{V_{reflected}}{V_{incident}} = \frac{V_L^- e^{-j\beta d_{min}}}{V_L^+ e^{j\beta d_{min}}} = \Gamma_L e^{-j2\beta d_{min}} = |\Gamma_L|e^{j\theta_L}e^{-j2\beta d_{min}}$$

Phase term should be $-\pi$. So $\theta_L = 2\beta d_{min} - \pi$

Experiment Setup

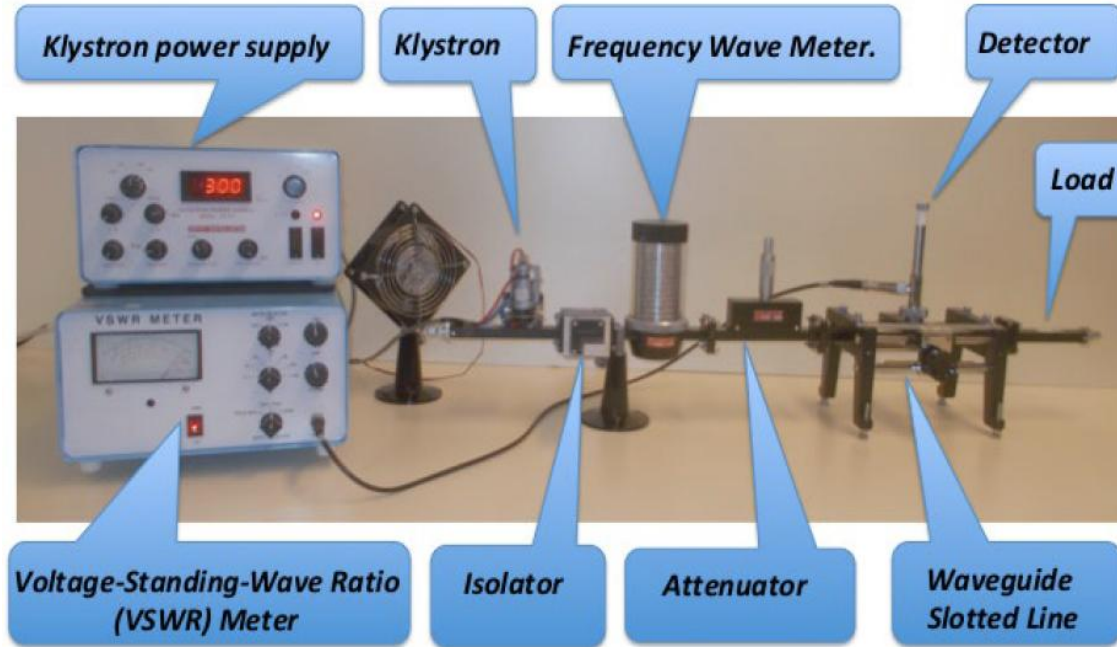

Summary of experiment procedure;

1. Determine operating frequency of the source using Frequency wave meter
2. Calibrate VSWR meter by sliding probe on slotted line
3. Measure VSWR values of different loads (open, matched load, antenna)
4. Measure VSWR values of short circuit under different piston locations